

Lecture - 1

Semi-conductor (অর্পণবিদ্যী)

insulator - অগ্রিবাহী

conductor - পরিবাহী

এইচু মাঝে semi-conductor
মাজের সংজ্ঞা

single crystal

negative temperature co-efficient - (inverse)

doping বেকুর semi-conductor এর conductivity
বৃদ্ধি বা কমানো যাব।

most used semiconductor material - Silicon, Germanium

Energy Level: (imp) v.v.

conduction level: current flow কৃত হয়,

পরম্পরা অমান্যম �semi-conductor insulator হয় শব্দ।
(ক্ষেত্রের ক্ষেত্র ক্ষেত্রের দ্রুত, energy level দিয়ে explain)# movement এক ইল নিচে যাব খেক পেতে পেতে গুরুত্ব
পূর্ণ না।

room temperature - 25°C

0 kelvin / -273.15° සිලිකෝන් ක්‍රිස්ටලය මැඟි

e⁻ pass තහවුරු room temp. - අ පිළි දෙනු

energy gain



breaking covalent band (මගුදාලු තුළුව)



Free electron



moveable electron


pentavalent - මෙය තුළුදාලු ප්‍රති තුළුවන - ප්‍රතිග්‍රීහ ප්‍රතිඵලි

anion (N-type)


trivalent - ප්‍රතියා ප්‍රතිඵලි (P-type)

Valence Band, Conduction Band, Forbidden Energy Gap.

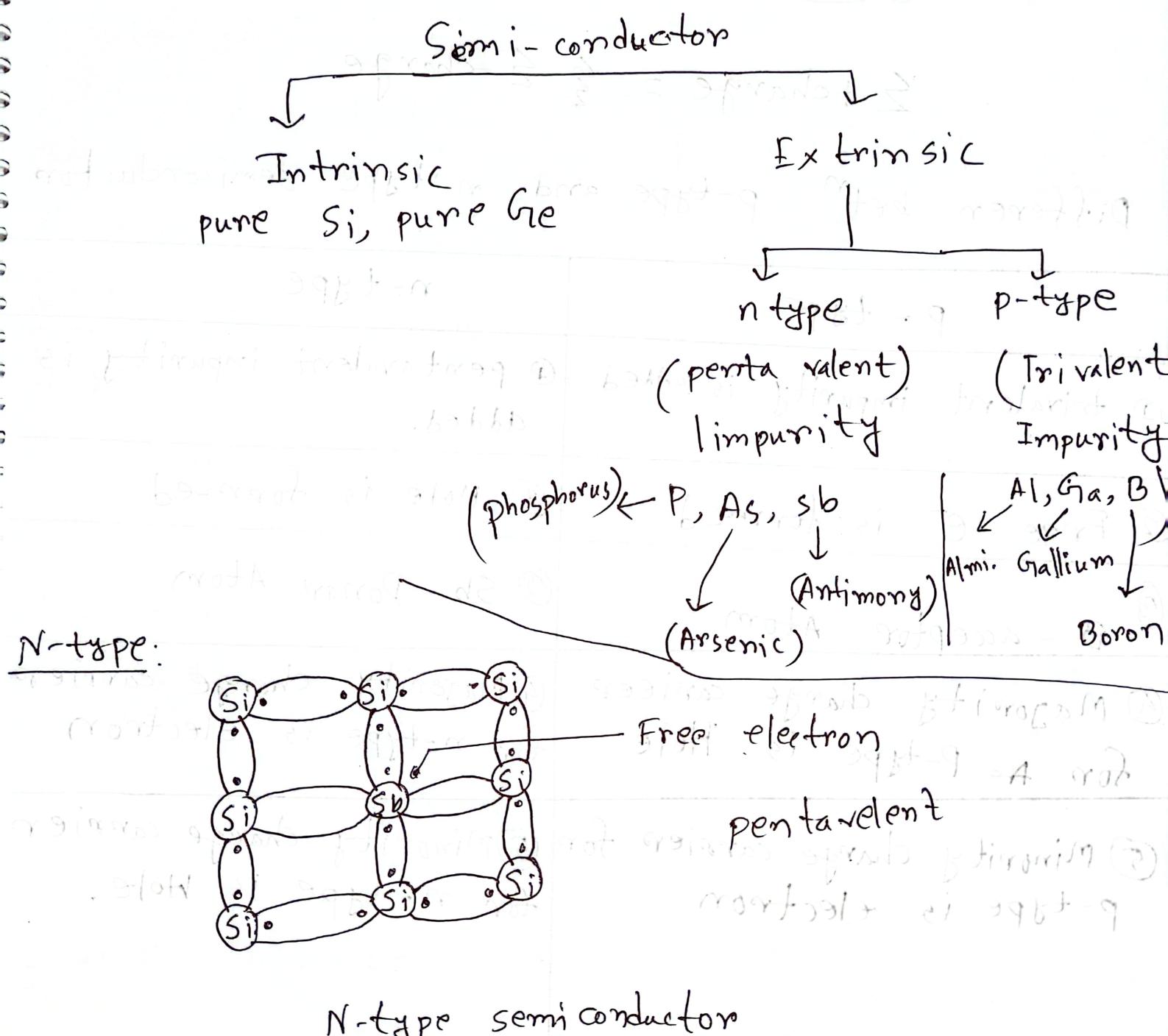Doping: The process of adding impurities to intrinsic semiconductors known as semiconductors.



P-type

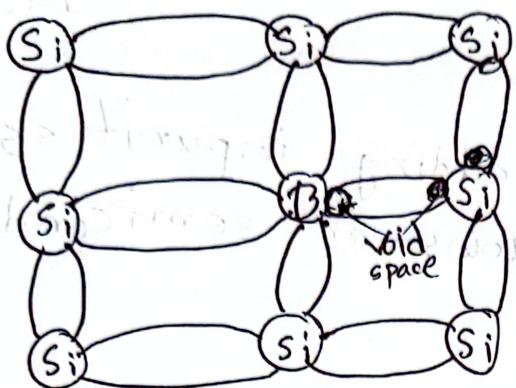




AL
Hole (state)

$$\Sigma +\text{charge} = \frac{1}{2} \Sigma -\text{charge}$$


Difference betⁿ p-type and n-type semiconductors

p-type	n-type
① trivalent impurity is added	① pentavalent impurity is added.
② Free e^- is formed	② Hole is formed
③ B - acceptor Atom	③ Sb - Donor Atom
④ Majority charge carrier for P-type is Hole	④ Majority charge carriers for n-type is electron
⑤ Minority charge carriers for p-type is electron	⑤ Minority charge carriers for n-type is hole.

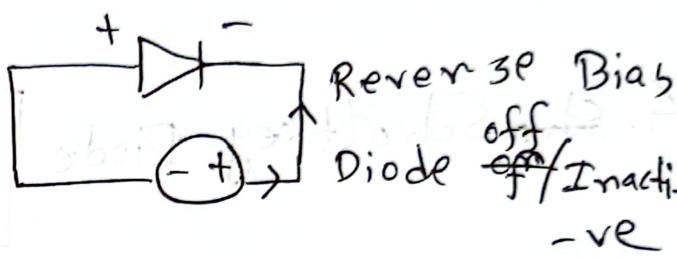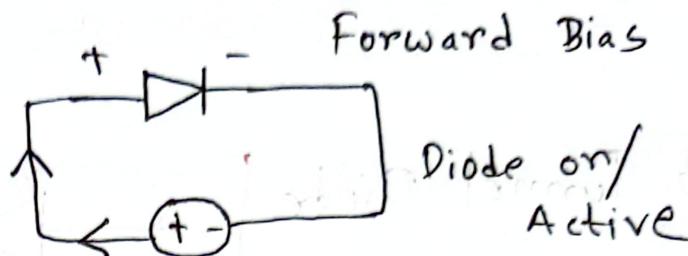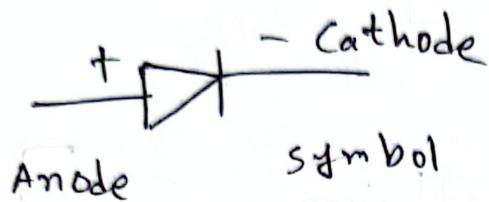Diode: Diode is a two terminal device that allows current to flow in only one direction and blocks current coming from opposite direction.



Rectifier:

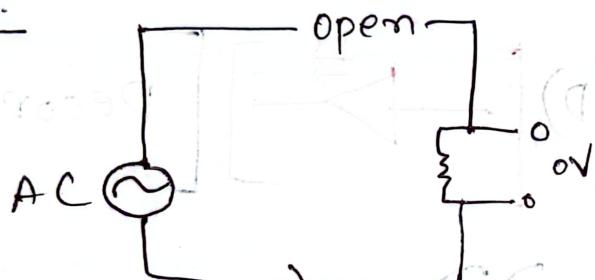

Lecture - 3, 4


EEE1231

25.08.2024

25.07.2024

Classification of Diode


1. p-n Junction diode/ rectifier

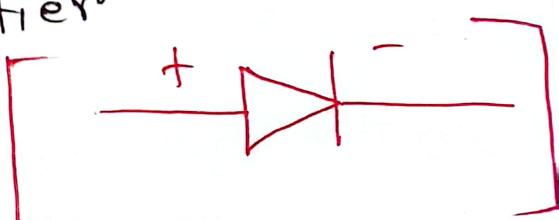

2. Zener Diode [stabilizer & voltage regulator স্টেবিলাইজার এবং ভৱেজার]




3. Tunnel Diode

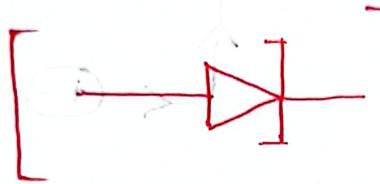


[switching
switching in PC]

4. Schottky Diode

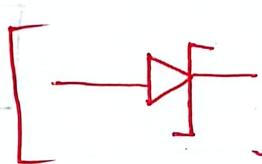


[high frequency and
high speed operation]

5. Light Emitting Diode (LED)

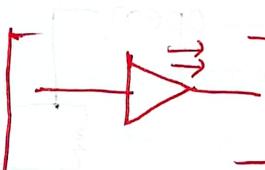


[Decoration]

6. photo Diode

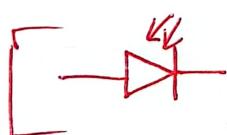

reciever



7. IR8 Diode

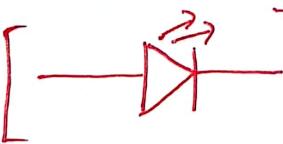


used as a pair in
pulse oximeter

transmitter

Internal Structure of Diode

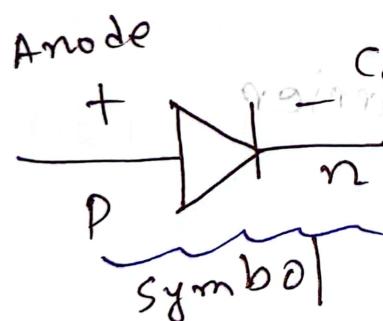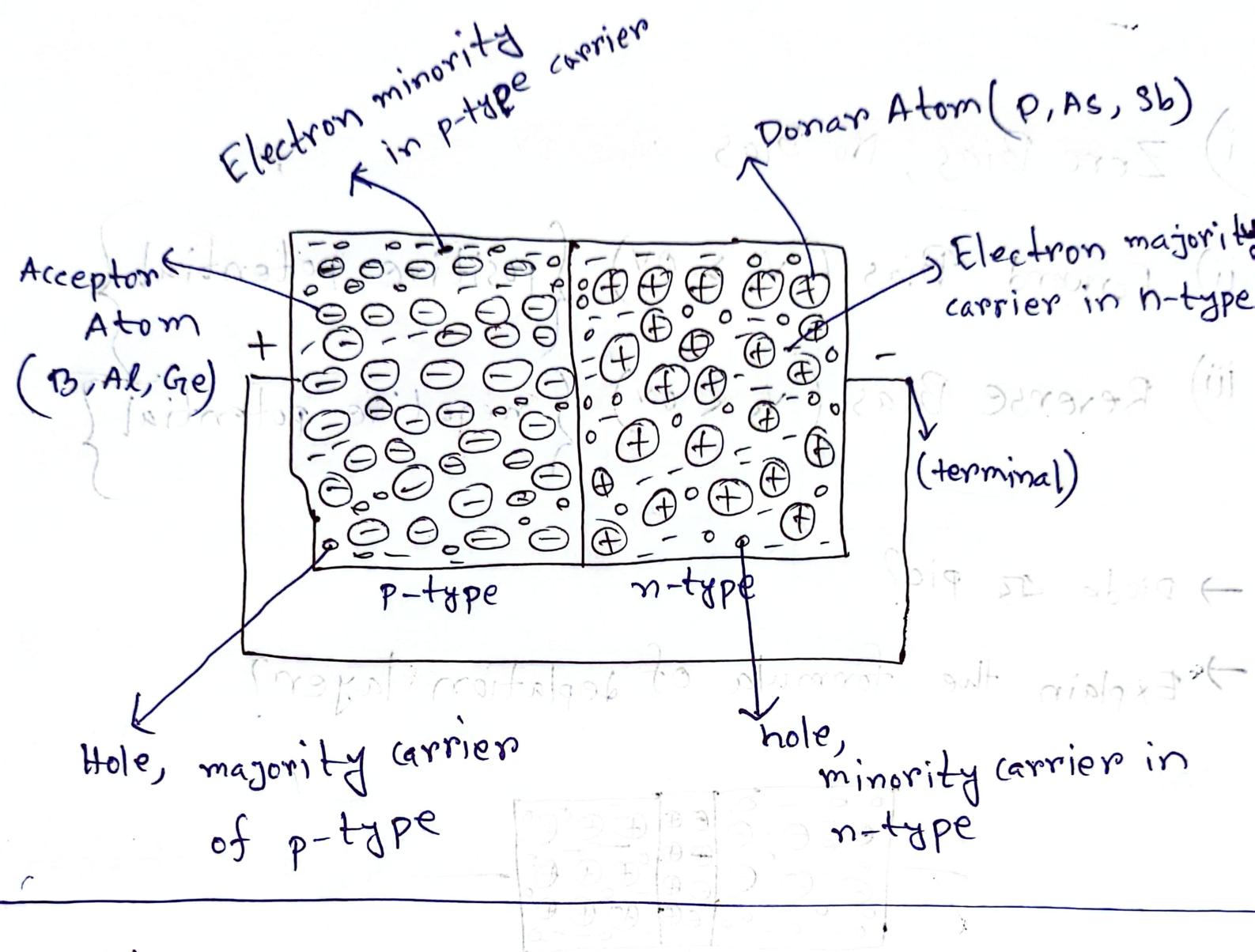

বাই: অতিপ্রযোগ্য একক্ষণীয়তা

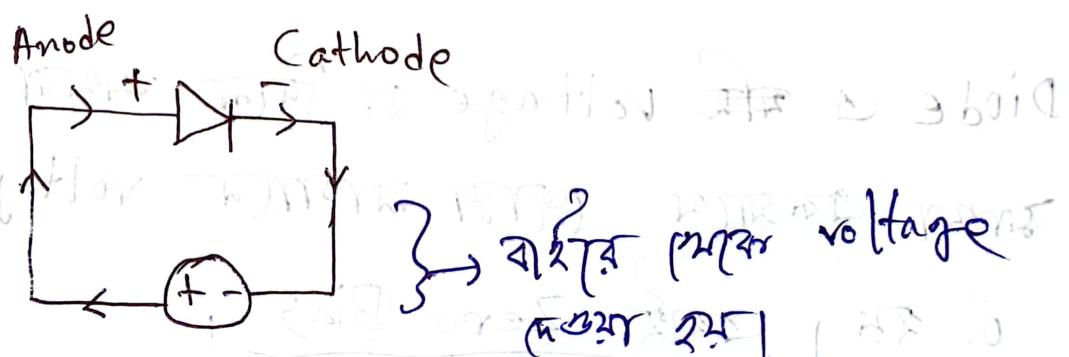

Biassing in Diode


i) Zero Bias, No Bias $V_s = 0V$

ii) Forward Bias ($V_s > 0V$) {positive potential}

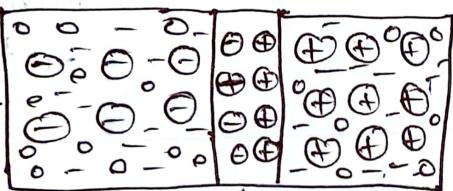iii) Reverse Bias ($V_s < 0V$) {negative potential}

→ Diode ഏ പി?

→ Explain the formula of depletion layer?




Depletion layer Barrier

i) Zero Bias

Diode എ ~~the~~ voltage നു ദില് അഥവ കൂടിയിൽക്കുണ്ട് എന്നേർ
മാറ്റുപ്പെടുമ്പോൾ ജോഡ് ലാഗാൻ voltage 0 എംബ current
0 ദില് | പ്രാഥ്മിക Zero Bias

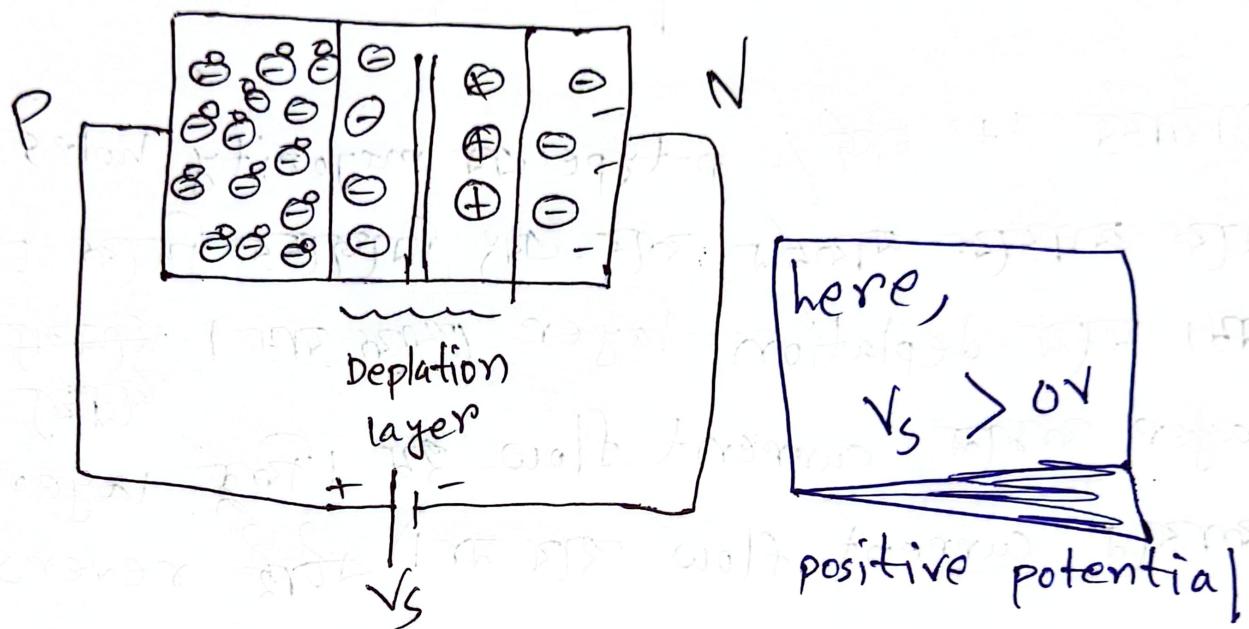ii) Forward Bias:

Diode - এব় (+) প্লাটের মাধ্যমে কার্ডিভ '+) প্লাট ও Diode
 এব় (-) প্লাটের মাধ্যমে কার্ডিভ '(-) প্লাট মুক্ত হয়ে।




Depletion layer মধ্যে জন্মে current flow

p-n junction \rightarrow forward Bias \rightarrow সূচী current flow

ব্যবহা

iii) Reverse Bias:

এখন, $V_s < 0V$

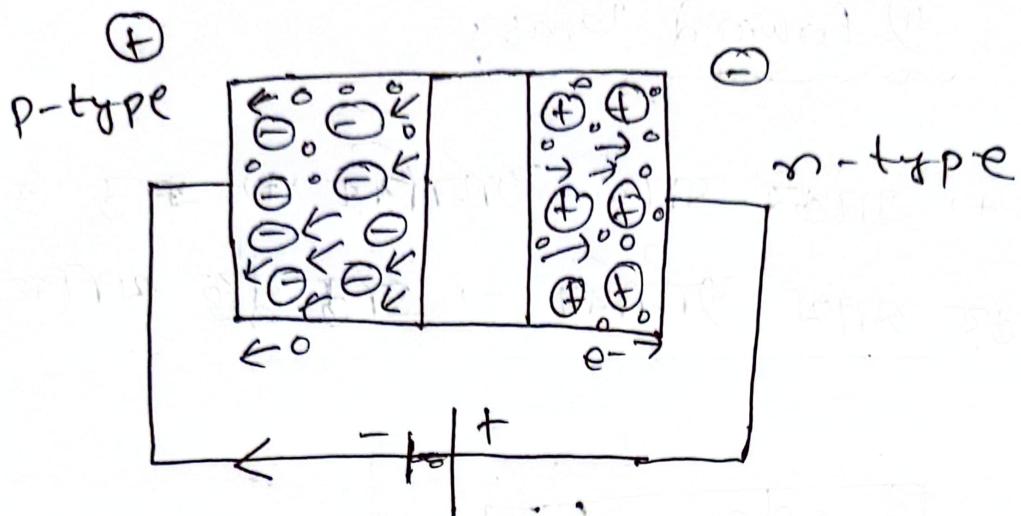

বাটারির '+' চৰ্দ / - p-type এৰ majority holes প্ৰচলিত।
 একে আবাবেক আকস্মাৎ কৰে এখন নিষিদ্ধ দ্বিতীয় চৰ্দ হৈন
 যেহেতু। ফলত depletion layer থাকিব। কৃতিক্ষম deplation
 layer কৰলে current flow হৈব। ফিল্ড layer কৰলে
 কাৰ্যকৰ current flow হৈব নহ। এটোৱা reverse bias.

p-n junction কৰ্ম : forward bias-এ কোণ কৰিব।

Graph of p-n junction diode with forward biasing

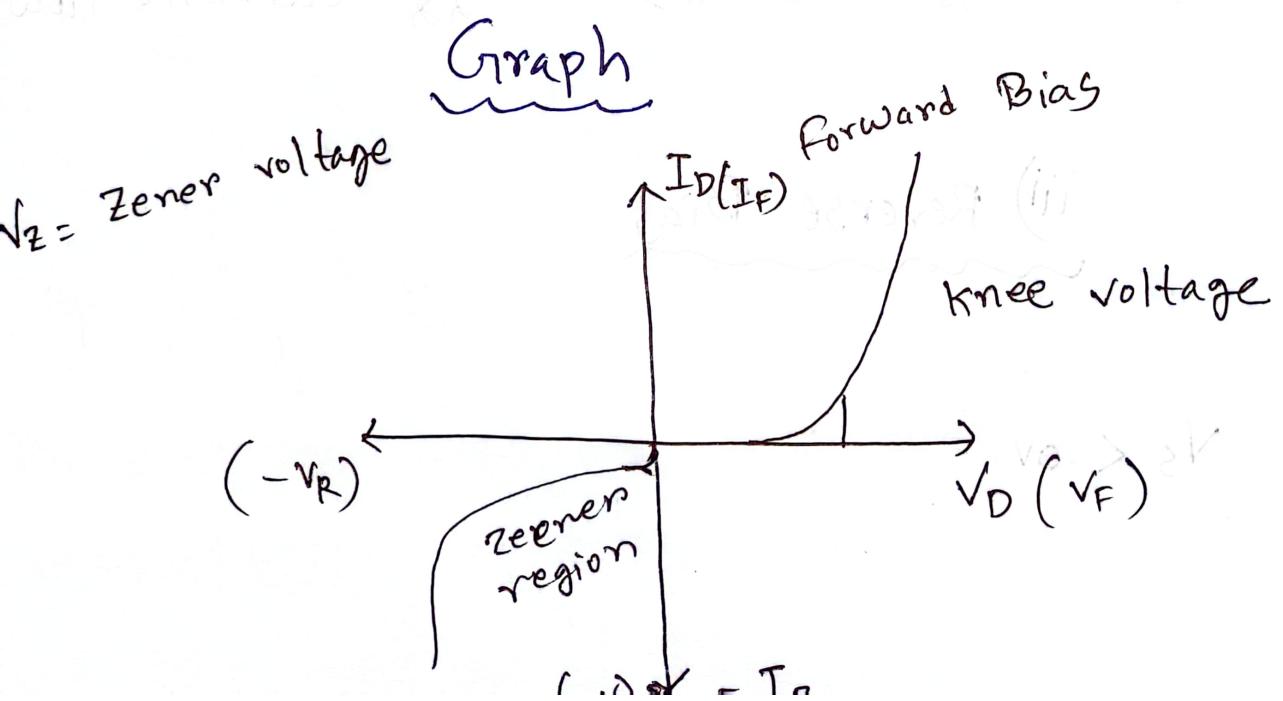


Fig: VI characteristic curve of a p-n junction knee voltage. The minimum amount of voltage for which current through a diode starts rising rapidly.

minority charge carrier depends on temperature
that's why ^{through} reverse bias, minority current does flow.

Zener reverse diode (मात्र बिट्टा)

EEE 1232

Semiconductors

Lecture-5
1-9-2024

Effect of temperature on Ge Diode

$$1. \left\{ \begin{array}{l} 200^\circ C \rightarrow Si \text{ (P-n)} \\ 200^\circ C \rightarrow Ge \text{ (Zener)} \end{array} \right.$$

$$2. \left\{ \begin{array}{l} \text{Breakdown voltage } Si = 2000V \\ Ge = 400V \end{array} \right.$$

$$3. \left\{ \begin{array}{l} \text{Silicon is more available and cheap than Ge} \end{array} \right.$$


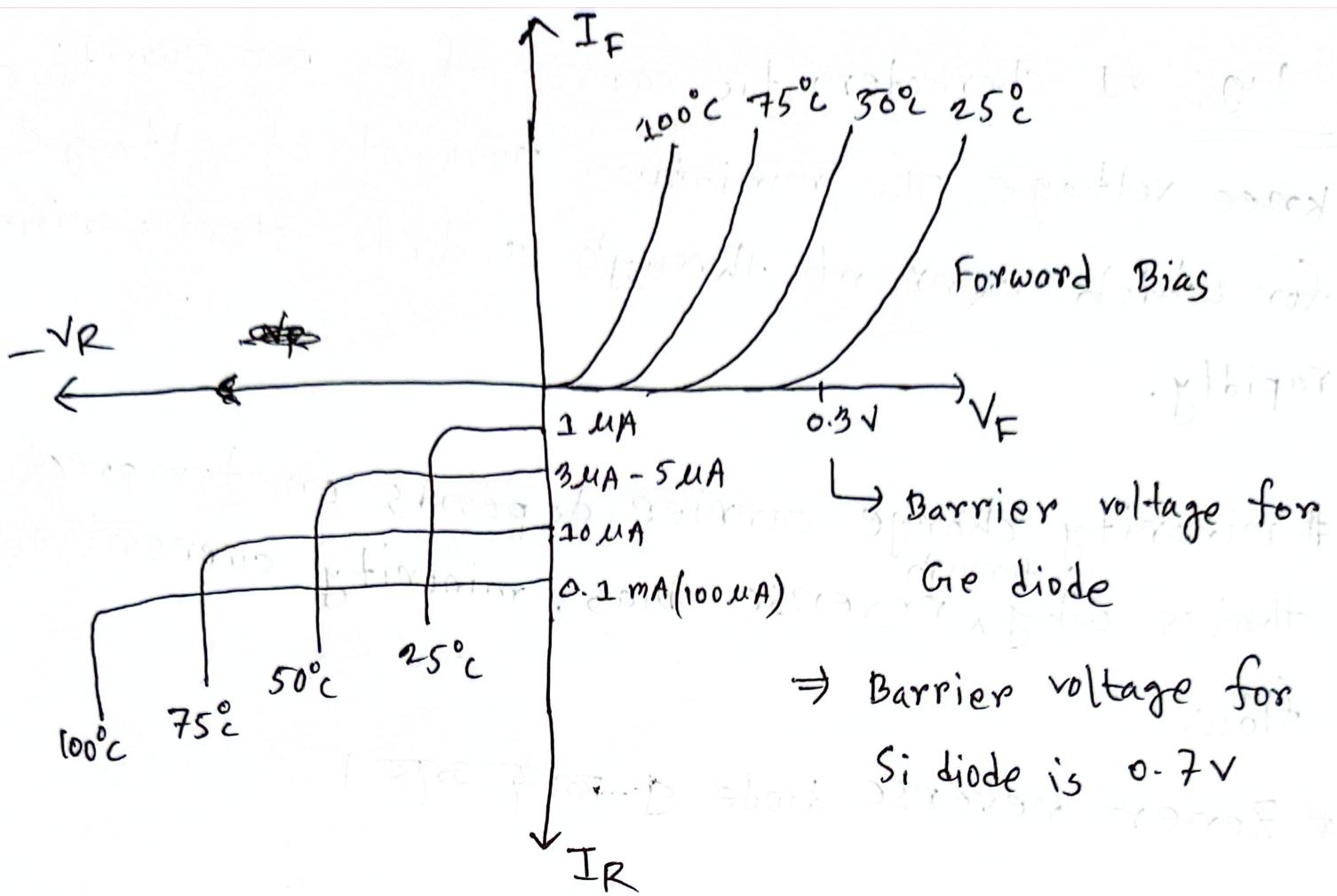


Fig : 1.24 (Book)

With the increase of temperature forward bias characteristics for of a Ge diode becomes more ideal

Math Part

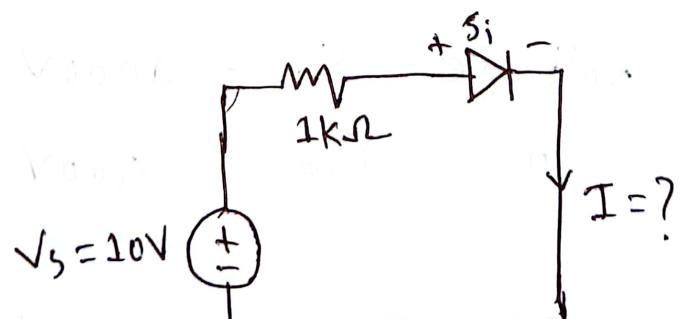

equivalent circuit
 $r_{in} = 0.7$


and result given for solution draw a graph

Two condition:

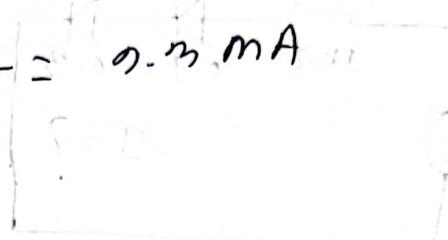1. Supply voltage, $v_s > 0.7$?
2. Diode ~~is~~ direction forward bias?

method - 1:

$$I = \frac{10 - 0.7}{1\text{k}\Omega} = 0.3 \text{ mA}$$




method - 2: Applying KVL,


$$-10V + v_R + 0.7 = 0$$

$$\text{or, } -10 + I \times 1 + 0.7 = 0$$
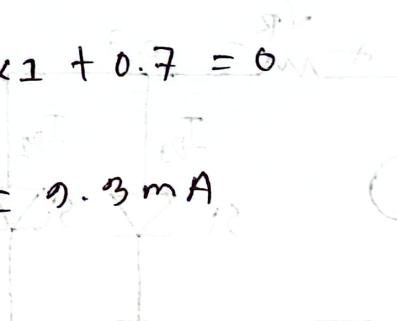
$$\text{if } I = \frac{10 - 0.7}{1\text{k}\Omega} = 0.3 \text{ mA}$$



Type: 2

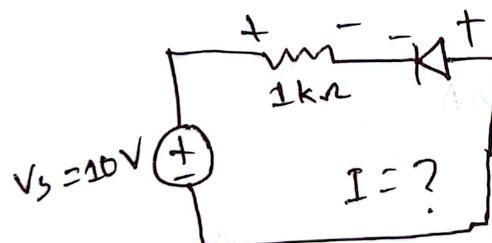


Hence diode is attached in opposite direction with v_s , that's why it is an open circuit.

$$\therefore I = 0$$

Type-3

$$V_s = 0.5 \text{ V}$$

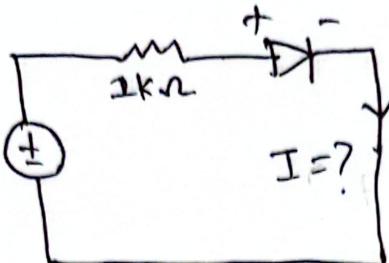


$$V_s < 0.7$$

So... diode will not active, Hence $V_s < 0.7$

Type-4

$$V_s = 10 \text{ V}$$

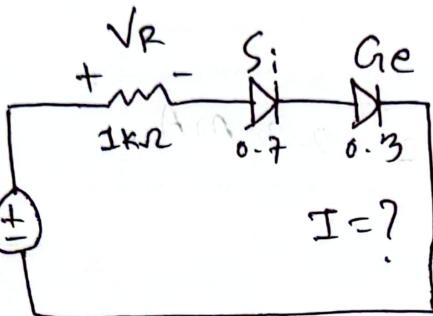


$$\therefore I = \frac{10 - 0.7 - 0.3}{1 \text{ k}\Omega}$$

$$= 0 \text{ mA}$$

Type-5

$$V_s = 20 \text{ V}$$

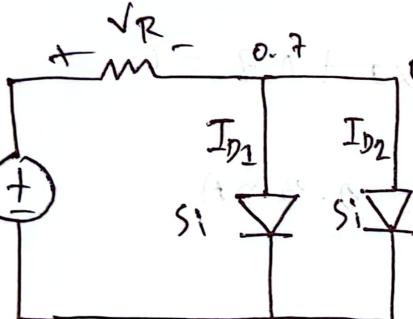


Calculate I, I_{D1}, I_{D2}

Here, $I = \frac{20 - 0.7 - 0.7}{1 \text{ k}\Omega} = 18.6 \text{ mA}$

Now, $I_{D1} = I_{D2} = \frac{I}{2} = 9.3 \text{ mA}$

Type-6

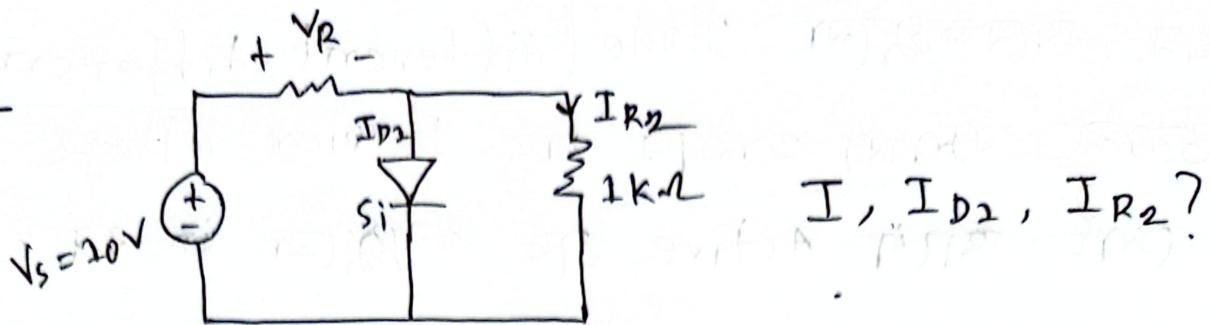

Here, $I = \frac{10 - 0.7}{1} = 9.3mA$

$$V = IR$$


$$I_{R2} = \frac{V}{R} = \frac{0.7}{1} = 0.7mA$$

Applying, KCL, $I = I_{D1} + I_{R2}$

$$\text{or, } I_{D1} = (9.3 - 0.7)mA$$

$$= 8.6mA$$

Type-7

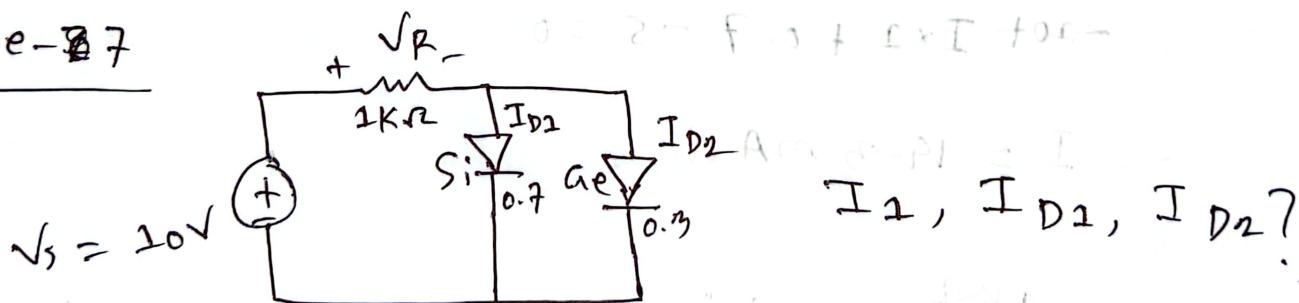

এখন, Ge এর voltage 0.3V হলে Ge এর diode

ইন্টার্স্যুর্স active হবে, $I = I_{D2} = \frac{10 - 0.3}{2} = 4.7mA$

$$I_{D2} = 0$$

$$\therefore I_{D2} = 0.7mA$$

ଯଦ୍ବା ଅନେକତାରୀ Diode (different different)
ଯାତ୍ରାର ସମ୍ବନ୍ଧ ଖଲୁ ମାତ୍ର barrier voltage ଯଳିବା
କିମ୍ବା ଓଟି ଆଗ୍ରା ଏବେ ଅନେକତାରୀ କି ବସି ଥିଲା



EEE 1232

Math Part

Lecture-6

02.09.2024

Q.1

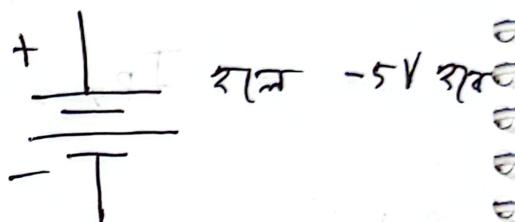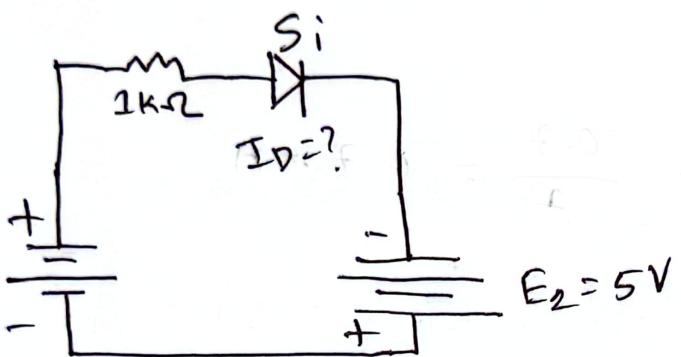


$$I = \frac{20 + 5 - 0.7}{1} = 19.3 \text{ mA}$$

Applying KVL,

$$-20 + I \times 1 + 0.7 - 5 = 0$$

$$\therefore I = 19.3 \text{ mA}$$


Q.2

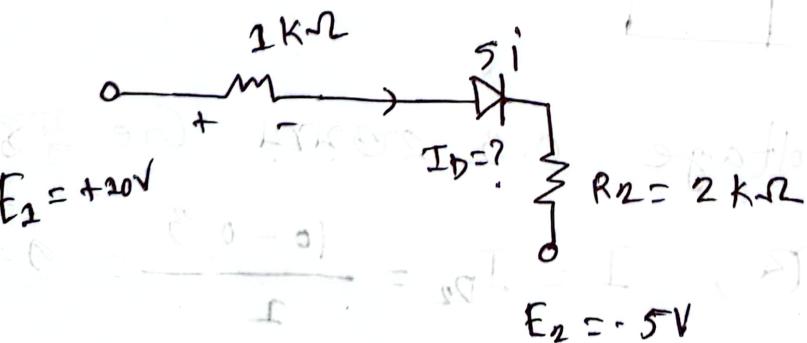

$$A = R_2 = \frac{20 - 0}{1} = 20 \Omega$$

$$A = R_2 = 20 \Omega$$

$$A = 20 \Omega$$

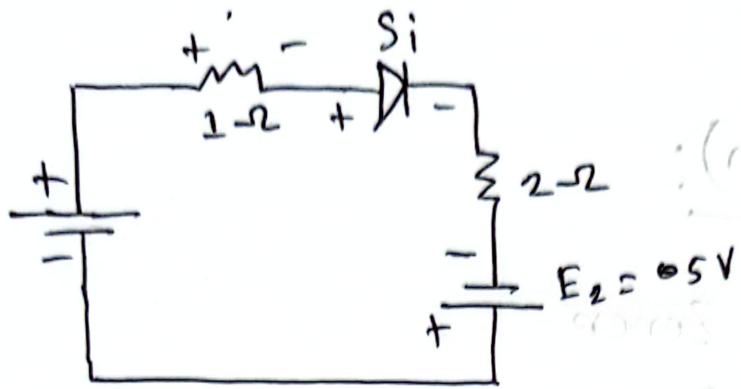

Applying KVL,

$$-20 + I \times 1 + 0.7 + 2 \times I - 5 = 0$$

$$\text{or, } I + 2I = 14.3$$

$$\therefore I = 4.767 \text{ mA}$$


Zener Diode

Sathya Chennai India

⇒ Heavily doped

⇒ Thin depletion layer

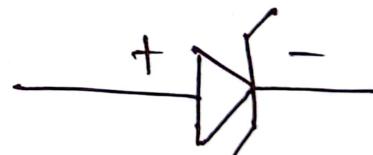⇒ $(1.8 - 200)\text{V}$ doping এবং পোর্ট ফিল্ড



symbol

⇒ 5.5V (জ্যাব মেট্রিক স্কেল)



মাত্র doping করণের উন্নত charge carrier বাড়ায়।

এবং depletion layer প্রতির শুধু মাত্র। এবং

Breakdown voltage ১৩৮২১

operation (3 region):

① In forward bias Zener

diode behave as a forward
p-n diode


② During reverse Bias $V_Z = 5V$,

when, $V_D < V_Z$, diode will be open circuited

③ During Reverse Bias

when $V_D > V_Z$, diode will work as a voltage

regulator.


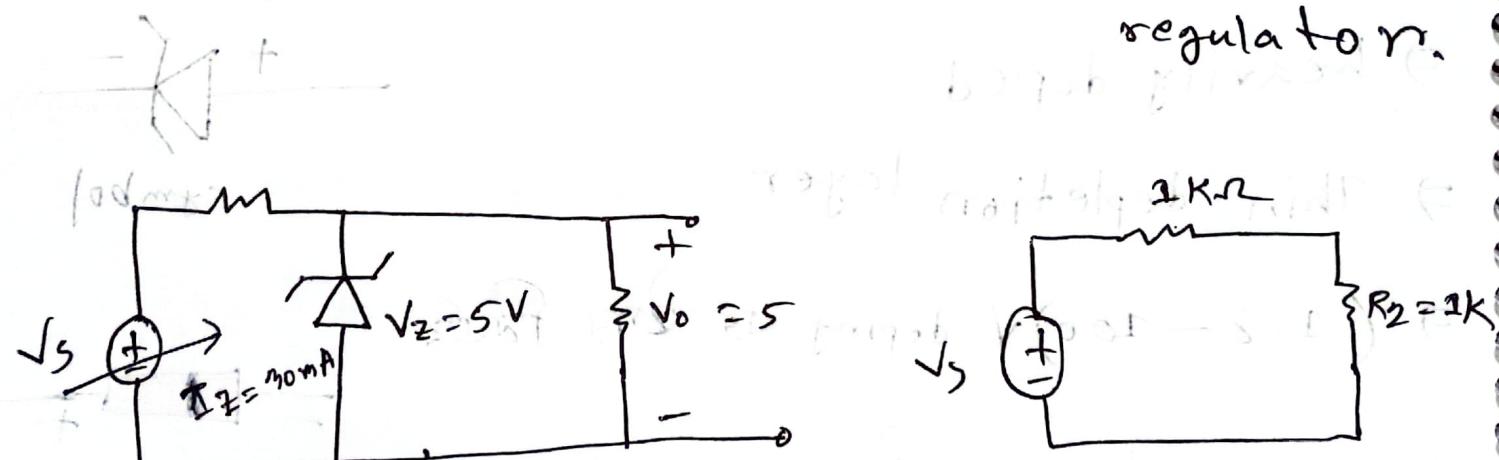


$$2V = V_{R_2} = \frac{1}{2+1} = \frac{1}{3}$$

$0.5 < V_Z$ circuit open

LED (Light Emitting Diode)

→ Emits light when energised.

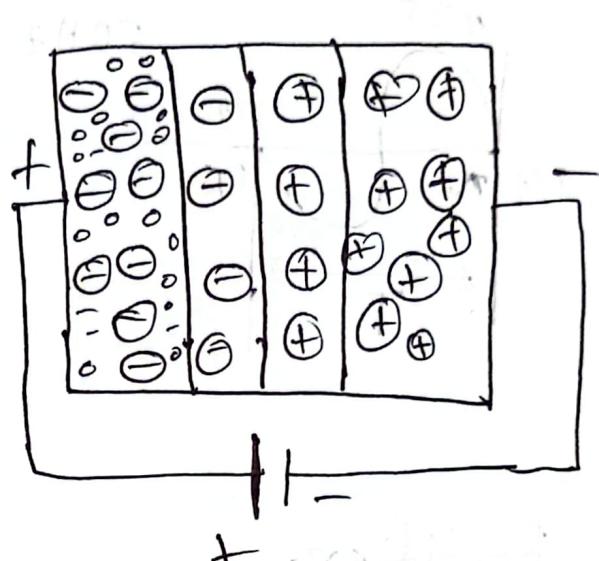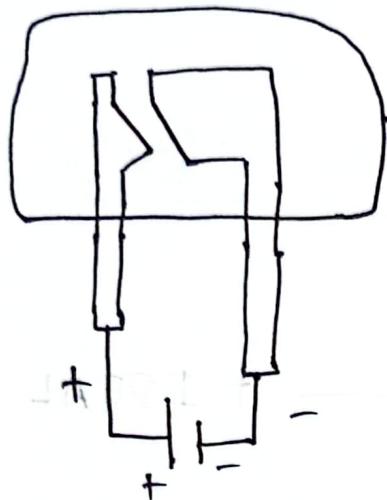

$$E_g = \frac{hc}{\lambda} \rightarrow 400 - 700 (\text{nm})$$

Materials → GaAsP, GaP

→ Define Electroluminescence?

EEE 1232

Lecture - 8

Application of Diode

09.09.2024

1. Rectifier circuit



2. clipper

3. clamper

} → wave shaping circuit


Rectifier

A device that converts AC into DC.

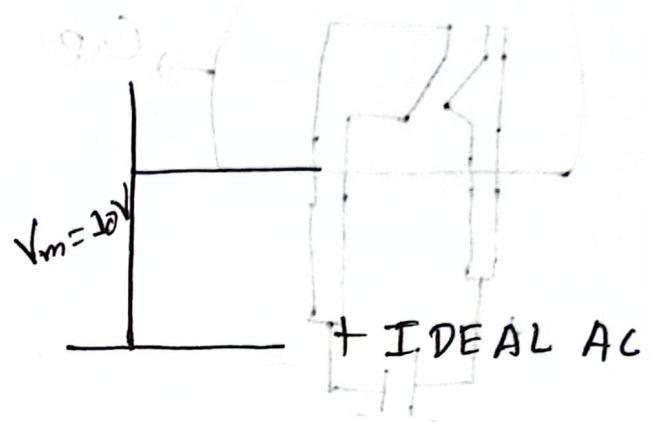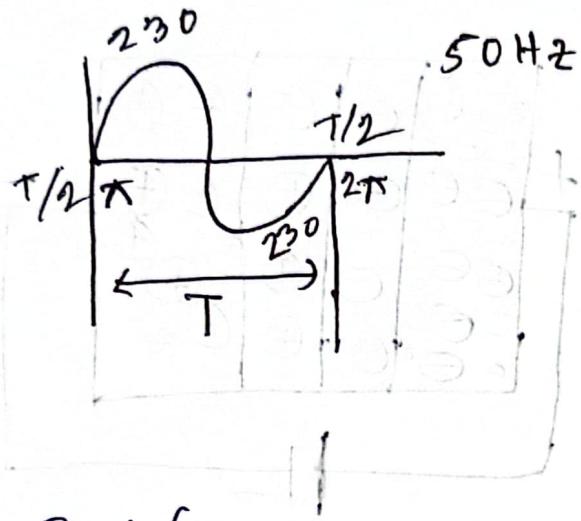

Types of Rectifier:

1. Half Wave Rectifier

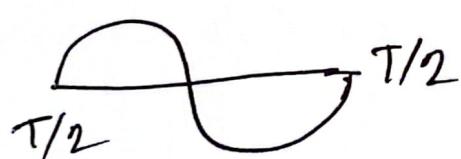



2. Full Wave Rectifier



Half Wave Rectifier

When diode positive,

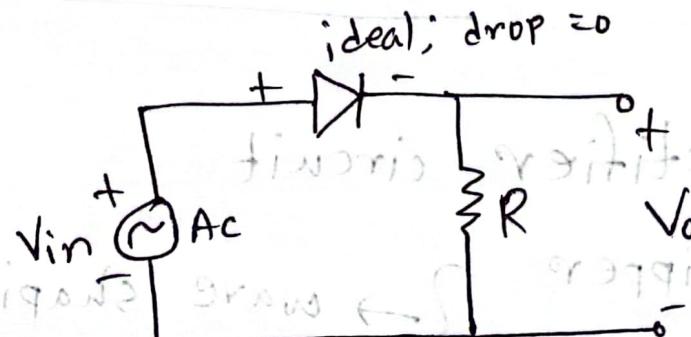


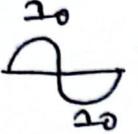
 During $\frac{(+)\text{ve}}{\text{source AC}}$ half,

Diode is active,



$$\therefore V_o = V_{in}$$

During $\frac{(-)\text{ve}}{\text{source AC}}$ half, diode is open

$$\therefore V_o = 0V$$

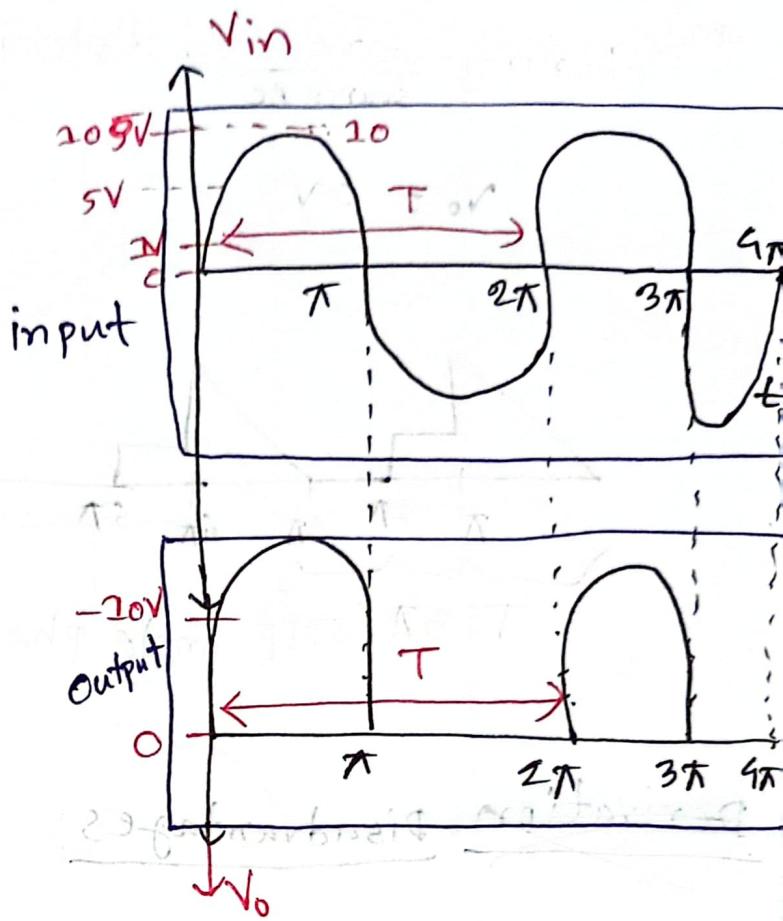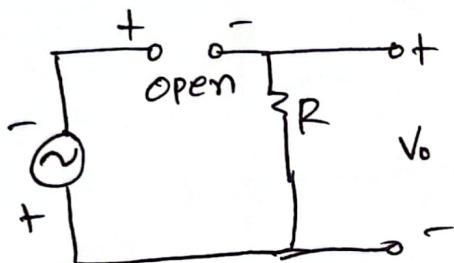

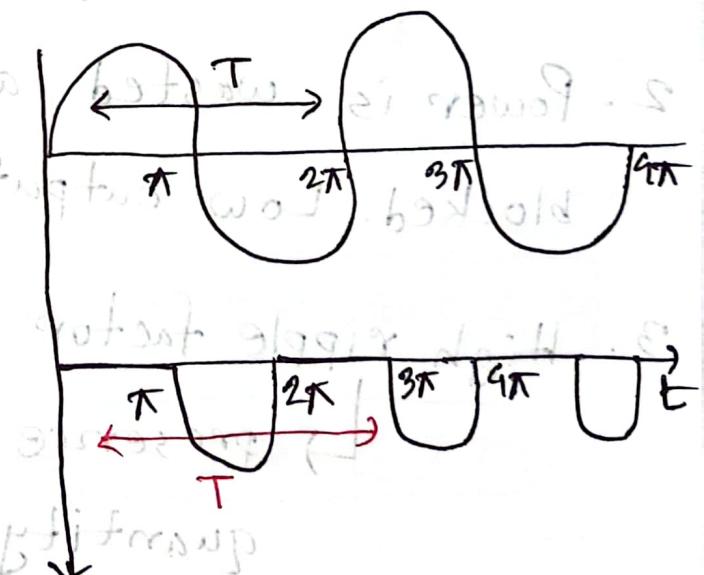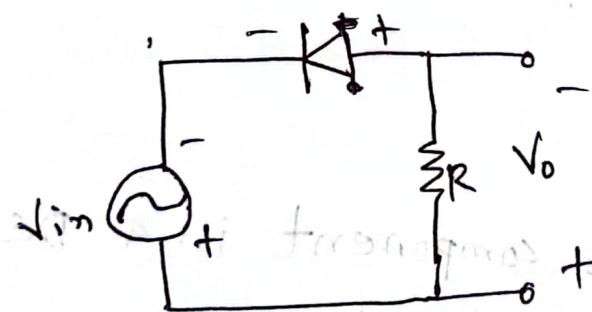During $\frac{(+)\text{ve}}{\text{source AC}}$ half, diode is negative,





During $\frac{(-)\text{ve}}{\text{source AC}}$ half, diode is active

$$T = 2\pi$$

$$\therefore V_{in} = V_o$$

and, During (+)ve source AC, diode is open


$$V_o = 0V$$

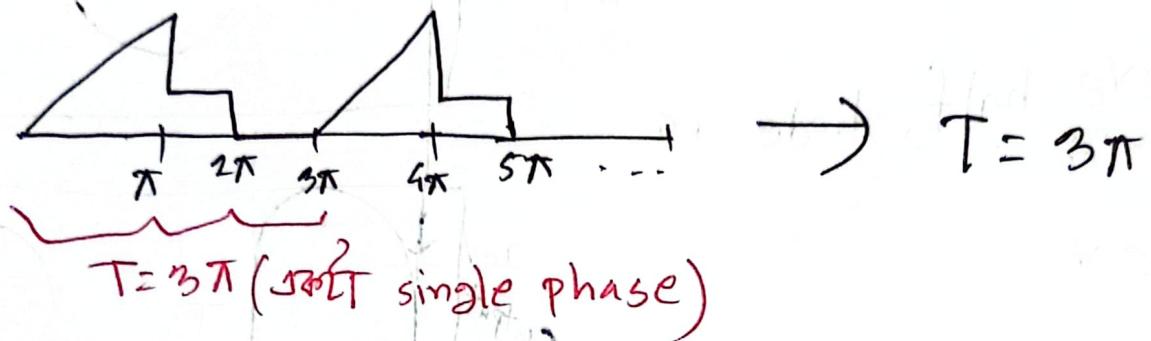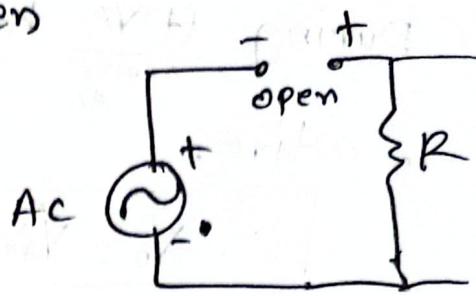

~~Derivation Disadvantages:~~

1. Low output voltage
2. Power is wasted as one of the half cycle is blocked. (Low output power.)
3. High ripple factor
 - ↳ presence of AC component in a DC quantity is called ripple.

Derivation:

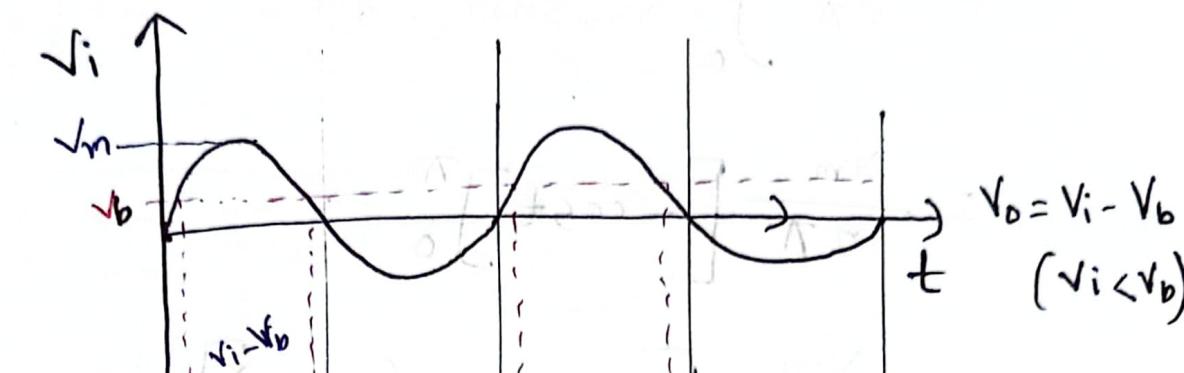


Ideal diode, V_0

$$V_0 = 0$$

$$V_0 = V_i \rightarrow +^{\text{ave}}$$

$$V_0 = 0 \rightarrow -^{\text{ave}}$$

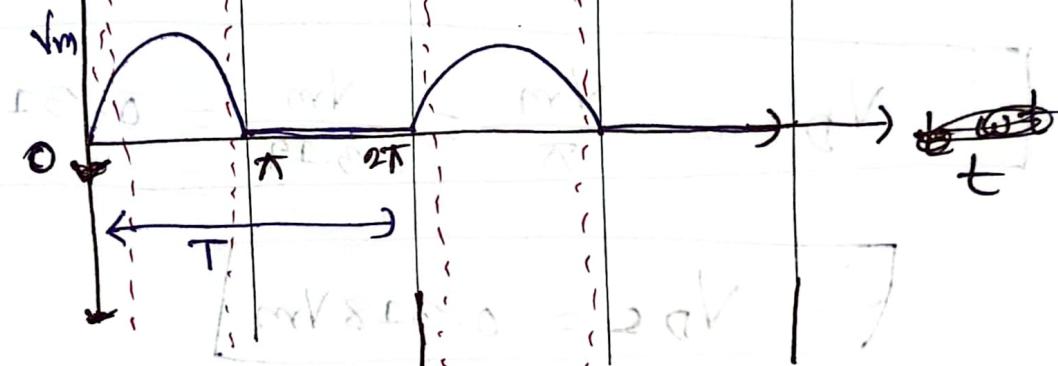

Output Voltage, (V_{DC})

$$V_0 = V_m \sin \omega t \rightarrow 0 \leq \omega t < \pi$$

$$\left[(+b) \right] + \left[(+b) \right] \rightarrow \pi \leq \omega t \leq 2\pi$$

$$\therefore V_{DC} = \int_0^{\pi} V_0 dt / \pi \quad [T=2\pi]$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} V_m \sin \omega t dt + \int_{\pi}^{2\pi} 0 \cdot dt \right]$$

$$= \frac{1}{2\pi} \int_0^\pi V_m \sin t \cdot dt$$

$$= \frac{V_m}{2\pi} \left[-\cos t \right]_0^\pi$$

$$= \frac{V_m}{2\pi} \left[-\cos\pi - (-\cos 0) \right]$$

$$= \frac{V_m \times 2}{2 \times \pi}$$

$$\therefore V_{DC} = \frac{V_m}{\pi} = \frac{V_m}{3.14} = 0.318 V_m$$

$$\therefore V_{DC} = 0.318 V_m$$

again, for, $V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_o^2 dt}$

$$[T = t_{end} - t_{start}] \quad \therefore T = \pi$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \left[\int_0^\pi V_m^2 \sin^2 t dt + \int_\pi^{2\pi} 0^2 dt \right]}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^\pi \sin^2 t dt}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left[\int_0^\pi \frac{1 - \cos 2t}{2} dt \right]} = \frac{V_m}{2\sqrt{\pi}}$$

$$V_{AC} = \sqrt{\frac{V_m^2}{2\pi}} \int_0^\pi \frac{1}{2}(1 - \cos t) dt$$

$$= \sqrt{\frac{V_m^2}{4\pi}} \left[t - \frac{\sin t}{2} \right]_0^\pi$$

$$= \sqrt{\frac{V_m^2}{4\pi}} \times (\pi - 0)$$

$$= \frac{V_m}{2}$$

$$\therefore V_{rms} = V_{AC} = \frac{V_m}{2}$$

extra

$$I_{DC} = \frac{V_{DC}}{R} = \frac{V_m/\pi}{R} = \frac{V_m}{R\pi} = \frac{I_m \times R}{R \times \pi}$$

$$\therefore I_{DC} = \frac{I_m}{\pi}$$

Similarly,


$$I_{AC} = \frac{V_{AC}}{R} = \frac{V_m/2}{R} = \frac{V_m}{2R} = \frac{I_m \times R}{2 \times R}$$

$$\therefore I_{AC} = \frac{I_m}{2}$$



PIV rating for Half Wave Rectifier

Lecture - 9
15.09.2024

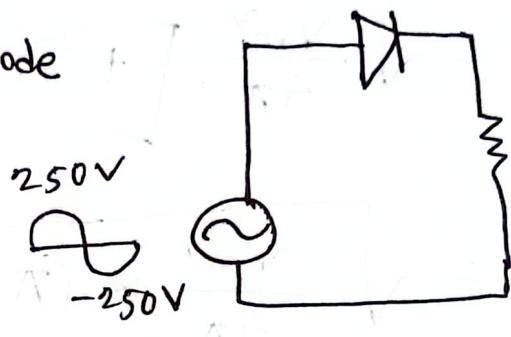मार्गिक या voltage फल Diode
रहे इधर ना तरी PIV rating



During (-)ve half cycle diode is open

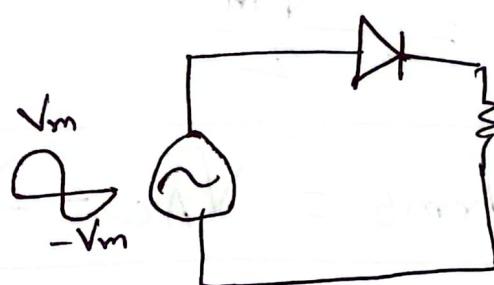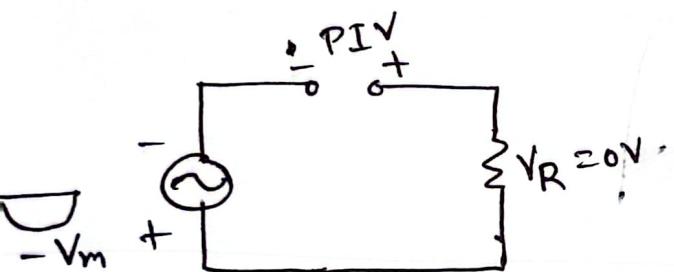


Applying KVL, $+V_m - PIV = 0$

$\Rightarrow PIV = V_m \rightarrow$ एवं Diode use करते ही
इधर या $PIV \geq V_m$ रहे

$$\frac{RI}{R+Z} = \frac{RI}{R} + \frac{RI}{R} \cdot \frac{Z}{R} = \frac{RI}{R} + \frac{IZ}{R} = IA + \frac{IZ}{R} = IA + \frac{I}{R} Z$$

$$\frac{mI}{R} = IA + \frac{I}{R} Z$$

Full Wave Rectifier

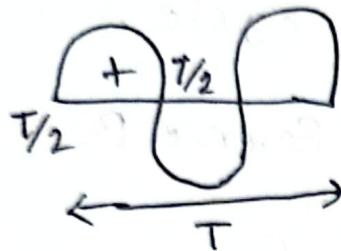


Types:

- 1 Full wave rectifier with centre tapped transformer
2. Bridge rectifier [4 diode] { ১ ব্রিজ একটি ফিল্ড সেল }

(2 diode কার্য)

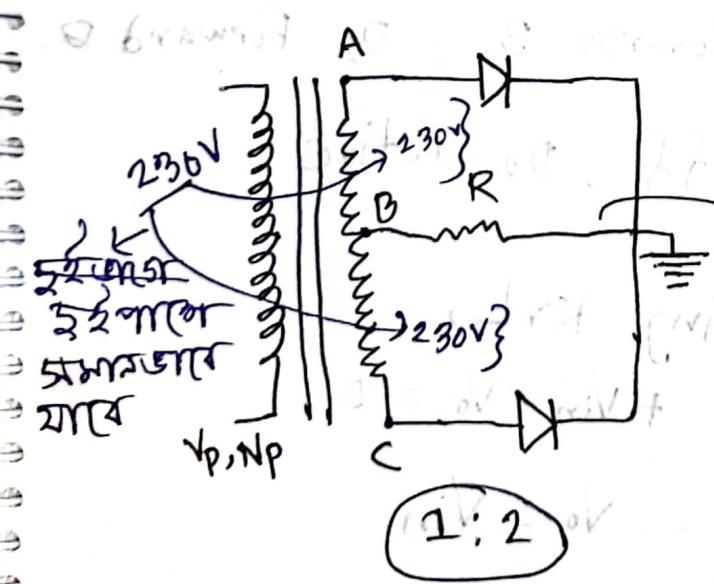Full Wave Rec with Centre-tapped Transformer




$$N_{AB} = N_{BC} \quad \left| \frac{V_p}{N_s} = \frac{N_p}{N_s}; V_p \propto N_p \right.$$

মাঝ (চুক্কি) wire করে
ground-এ কানক | ফাল
AB, BC কো অস আগ ইন্দ্র

1:2

For Positive half cycle

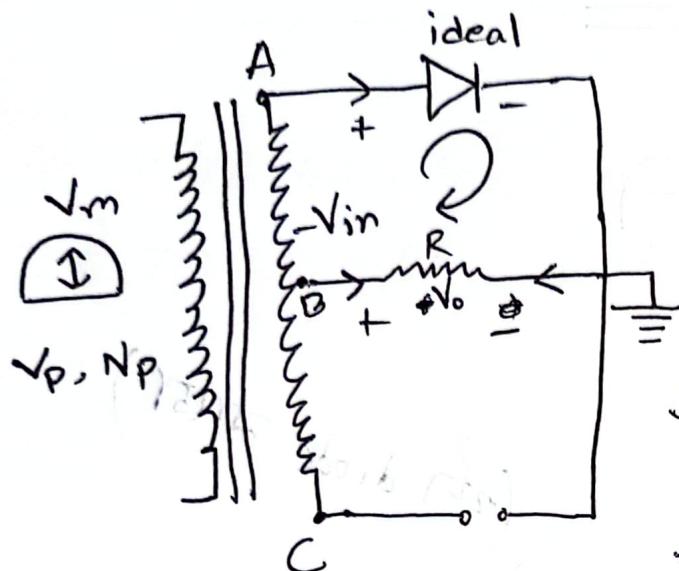


During (+)^{ve} half cycle,
D₁ Forward B., D₂ Reverse B.

∴ D₁ active, D₂ off

$$\therefore V_o = V_{in} \quad \left\{ \begin{array}{l} \text{applying KVL,} \\ -V_{in} + V_o = 0 \\ \therefore V_o = V_{in} \end{array} \right.$$

For Negative half cycle

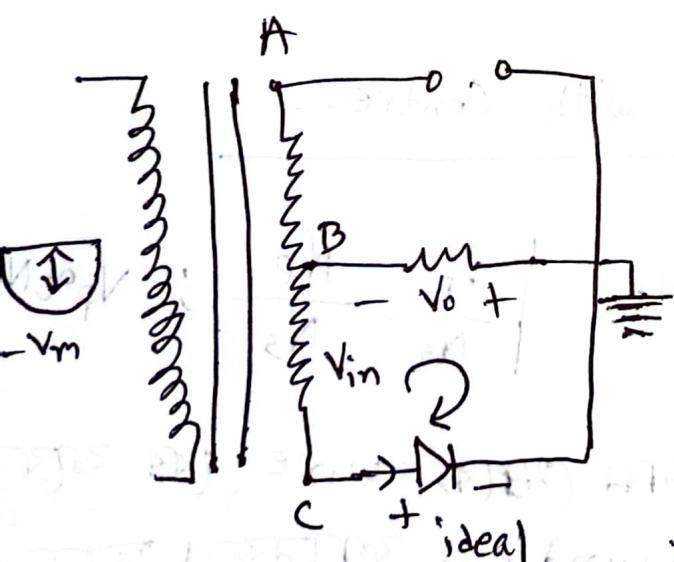

During (-)^{ve} half cycle


D₁ Reverse B., D₂ Forward D.

∴ D₁ off, D₂ active

∴ Applying KVL,

$$+V_{in} - V_o = 0$$

$$\therefore V_o = V_{in}$$


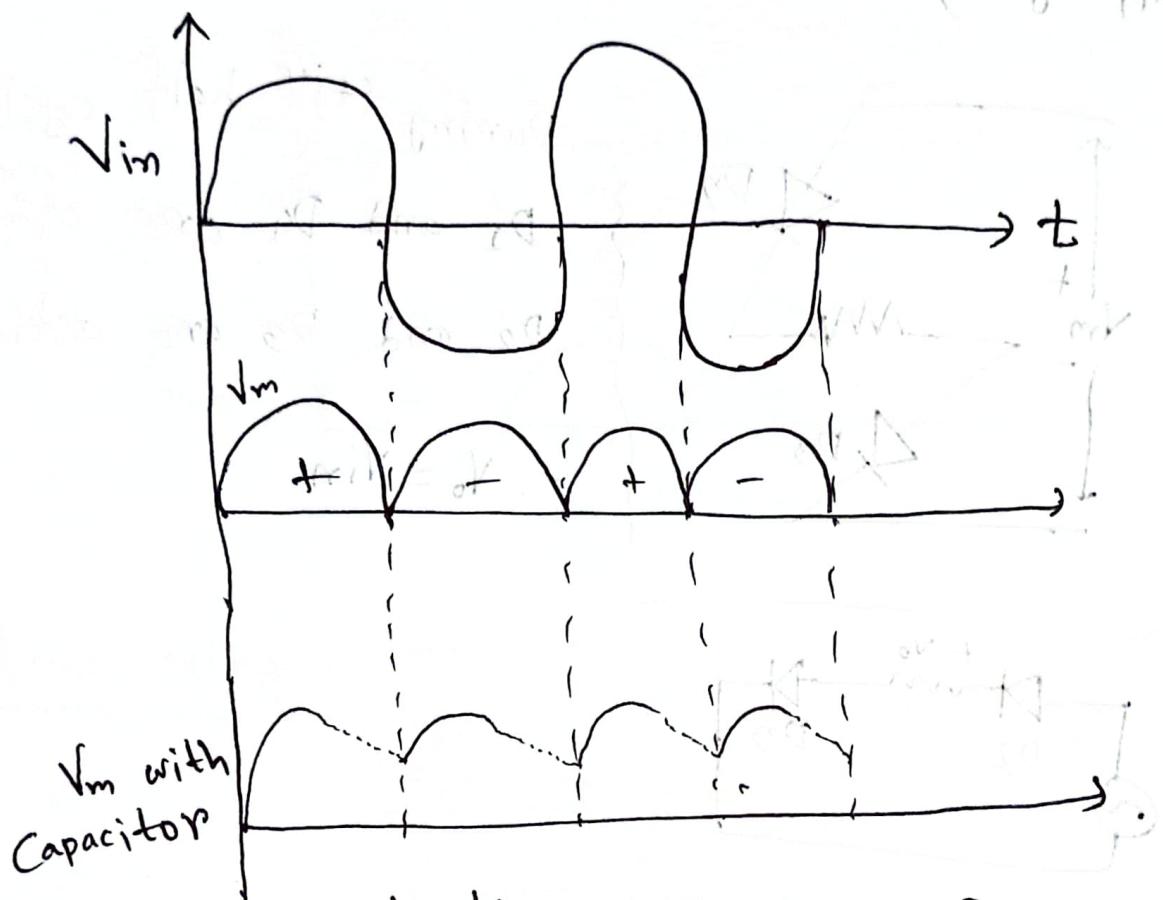


pulsating $D_c = A_c + D_c \}$ ripple factor


EEE 1231

** Bridge Rectifier


Lecture - 10
22.09.2024

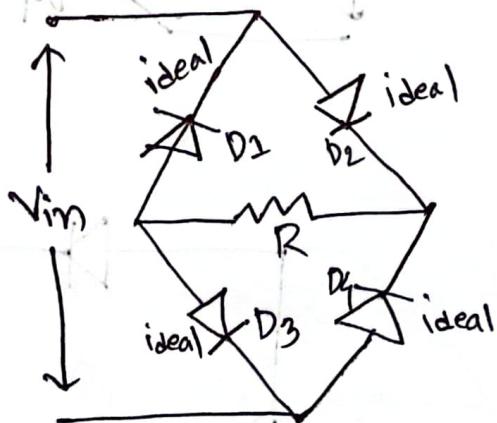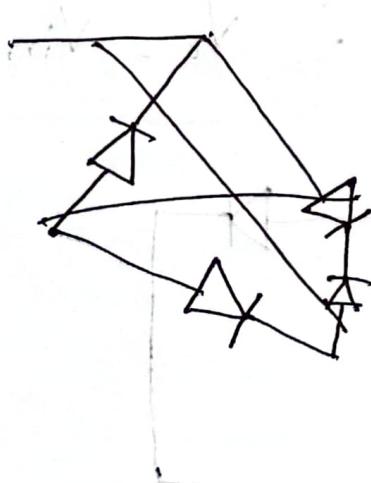

positive half cycle;

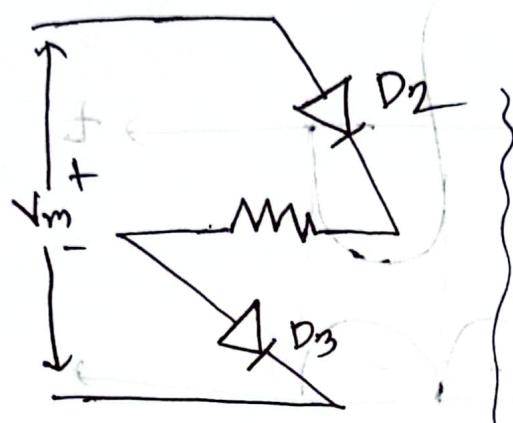


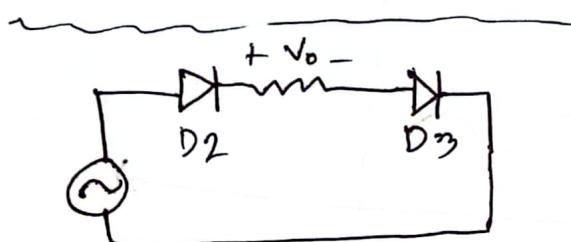During $(+)^{ve}$ half cycle
 D_2 and D_4 are off.
 D_2 and D_3 are active
 $\therefore V_o = V_{in+}$




negative half cycle { extra + 2A = 30 markings


negative half cycle,

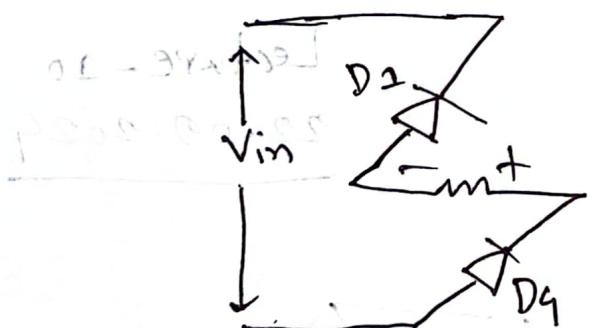

During $(-)^{ve}$ half cycle
 D_2 and D_3 are off.
 D_1 and D_4 are active

$$\therefore V_o = V_{in-}$$

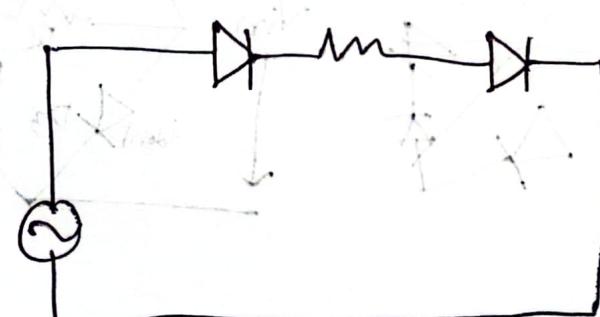

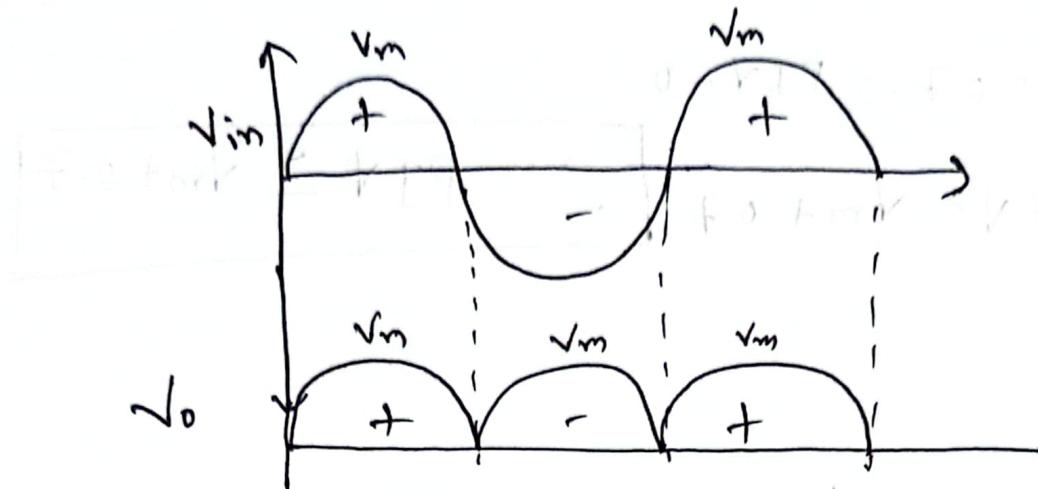

V_o = V_m

Output voltage:

$$V_{DC} = \frac{2V_m}{\pi}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

both bridge and centre tapped

centre tapped : $\rightarrow V_{DC} = \frac{2V_m - 0.7/0.3}{\pi L}$

bridge tapped : $\rightarrow V_{DC} = \frac{2V_m - 2 \times 0.7/0.3}{\pi L}$


PIV rating

when ideal diode,

$$+V_o - \phi \cdot PIV = 0$$

$$\Rightarrow PIV = V_o(\max)$$
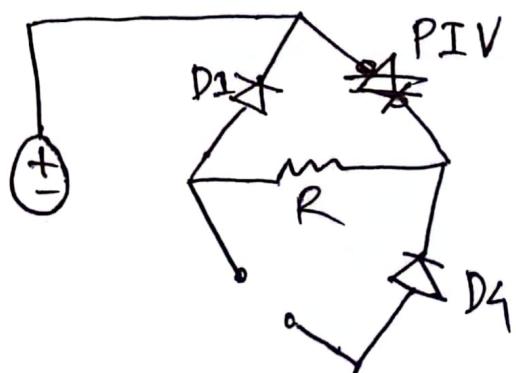
$$\therefore PIV = V_m \mid PIV \geq V_m$$






when Si diode,

$$+V_o + 0.7 - PIV = 0$$
$$\therefore PIV \leq V_m + 0.7$$


$$\therefore PIV \geq V_m + 0.7$$

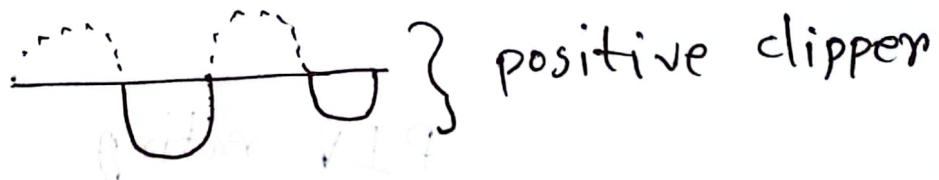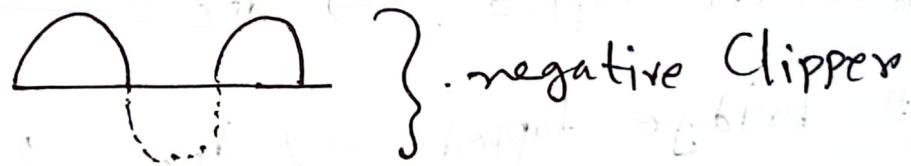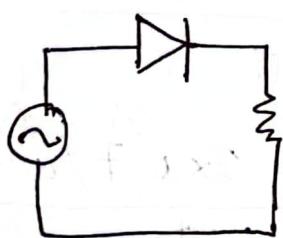* 2. Clipper

Clipper: Clipper is a device that clips off a portion of the input waveform without distorting the remaining part.



Type-1

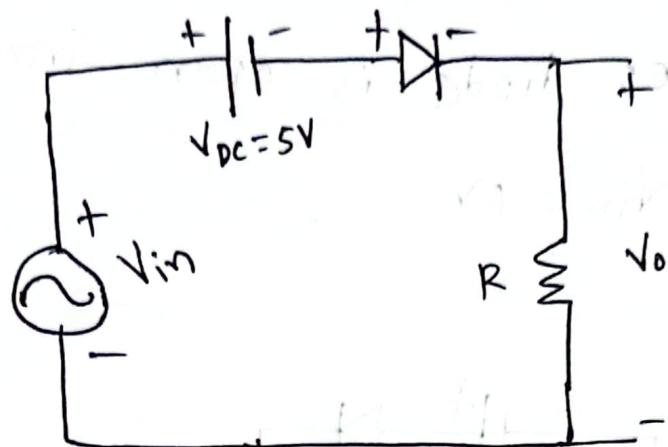

During (+)ve half cycle,

when $V_{in} < V_{DC}$

D_1 is off, so

$$V_o = 0V$$

when $V_{in} > V_{DC}$

Applying KVL, for Top branch


$$-V_{in} + V_{DC} + V_o = 0$$

$$\Rightarrow V_o = V_{in} - V_{DC}$$

$$\text{or, } 5 - 5 = 0V$$

$$\text{or, } 7 - 5 = 2V$$

$$\text{or, } 20 - 5 = 15V$$

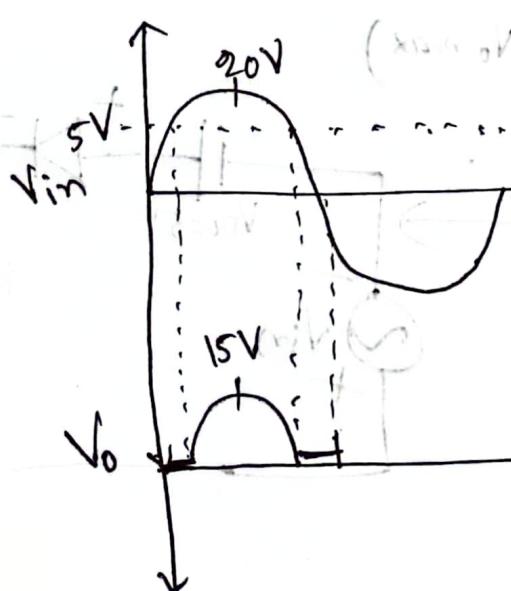

$30V > 20V$ results

$30V + 5V = 0V$


$$T = 2\pi f$$

$$f = \omega / 2\pi$$

and During $(-)^{ve}$ half cycle,
for both sources diode is open circuited,

$$V_{in} = 0V$$

Type-2

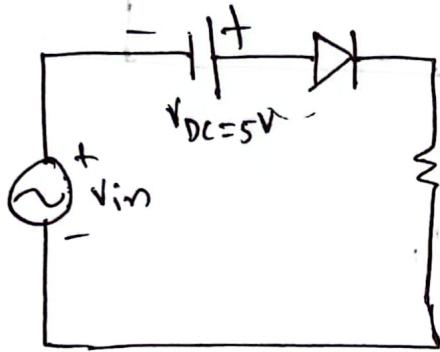

During $(+)^{ve}$ half cycle, both source diode is active

$$-V_{in} - V_{DC} + V_o = 0$$

$$\therefore V_o = V_{in} + V_{DC}$$

$$= 0 + 5 = 5V \quad (V_o \text{ min})$$

$$= 20 + 5 = 25 \quad (V_o \text{ max})$$

During $(-)^{ve}$ half cycle,


when $V_{in} < V_{DC}$

$$+V_{in} - V_{DC} + V_o = 0$$

$$\therefore V_o = -V_{in} + V_{DC}$$

$$= 0 + 5 = 5$$


$$= -5 + 5 = 0$$

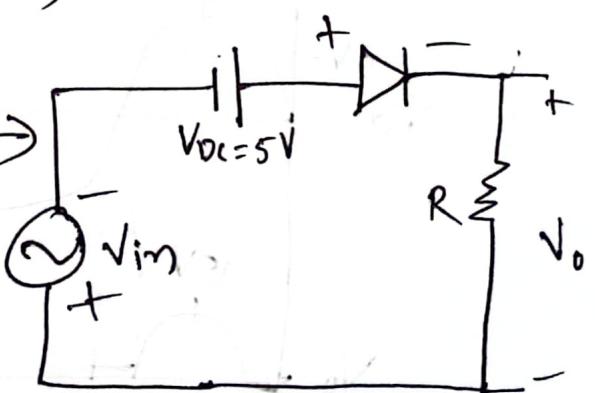

when $V_{in} > V_{DC}$, $D_0 - D_2$ (diode) is open.

$$\begin{aligned}\therefore V_o &= 0V \quad \text{if } V_{in} > V_o \\ &= -(5+5)V = 0V \\ \text{or, } &= (-4+5)V = 1V \\ \text{or, } &= (-2+5)V = 3V \\ \text{or, } &= (0+5)V = 5V\end{aligned}$$

Book → Biased series
clipper.


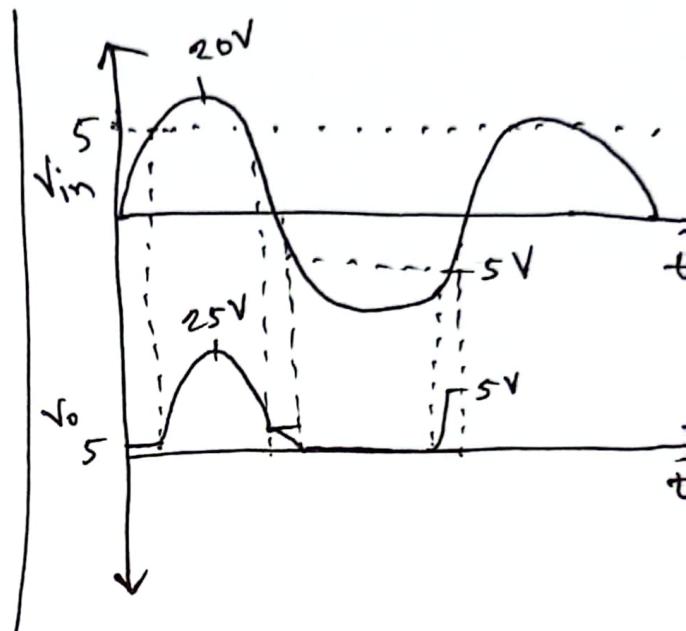


EEE 1232


Clipper Math

Lecture - 12

23.09.2024

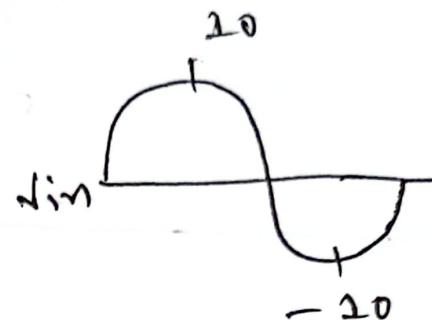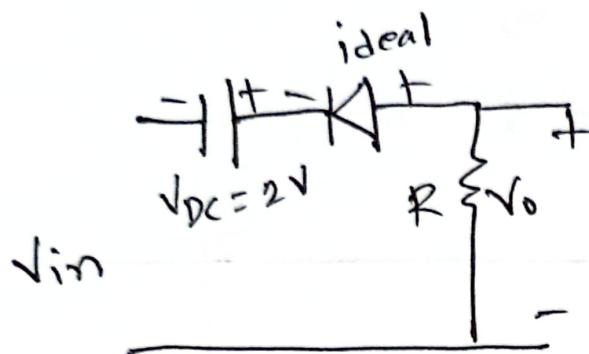


During $(+)^{\text{ve}}$. (half cycle),

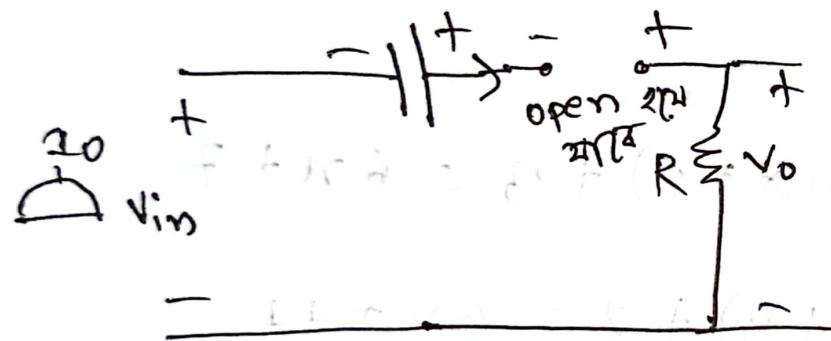

for both sources diode
is open,
 $V_o = 0V$

During (-)ve half cycle (negative)

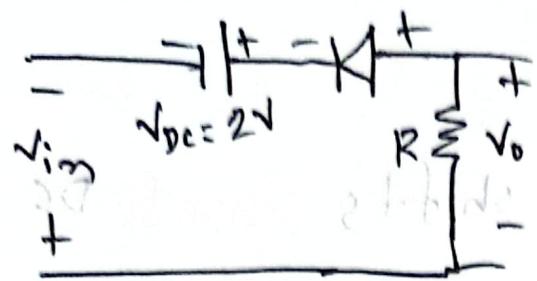

when $V_{in} < V_{DC}$,
diode open circuited

$$V_o = 10V$$


and, when $V_{in} > V_{DC}$

KVL,

$$+V_{in} - V_{DC} + V_o = 0$$

$$\therefore V_o = -V_{in} + V_{DC}$$
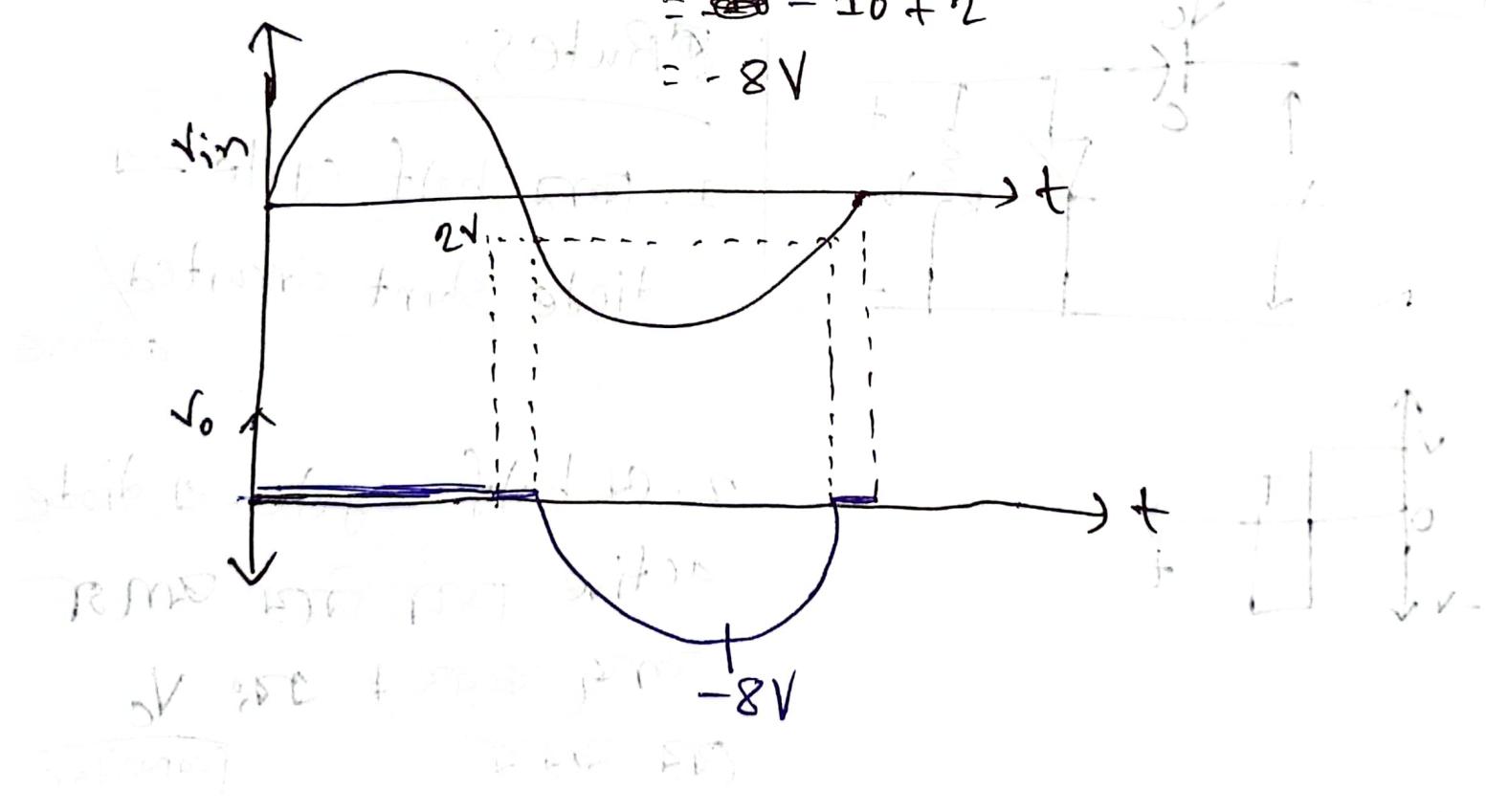
$$\begin{aligned} &= -20 + 2 \\ &= -8V \end{aligned}$$





and voltage different.


positive or negative?

Clamper

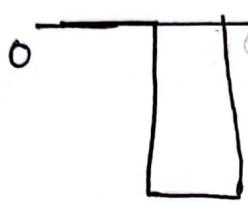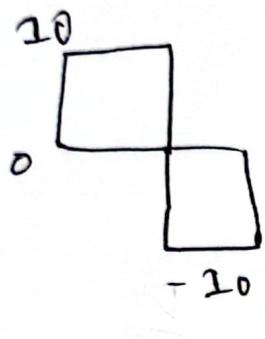→ Clamper is a circuit that shifts input DC level into another DC level.




Math-2

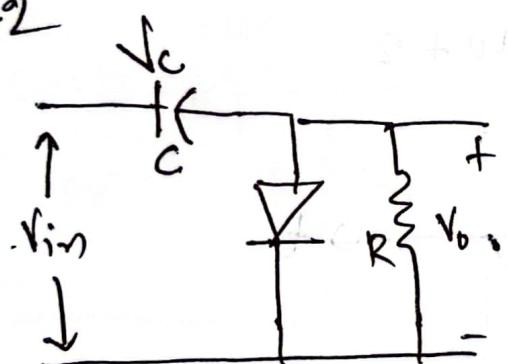

Rules:

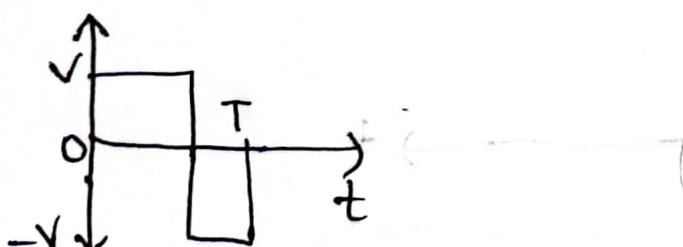1. ~~for half cycle -~~ diode short circuited/ active



2. ~~(V half cycle -) diode active~~ প্রথম সেকেন্ডে দালান করবে V_c

বের করবে v_o (capacitor)

3. finally other half cycle এর জন্য v_o বের করবে

for (+)^{ve} half cycle,


diode is active

$$V_o = 0V$$

$$\therefore -V_{in} + V_C = 0$$

$$\therefore V_C = V_{in}$$

$$= 20V$$

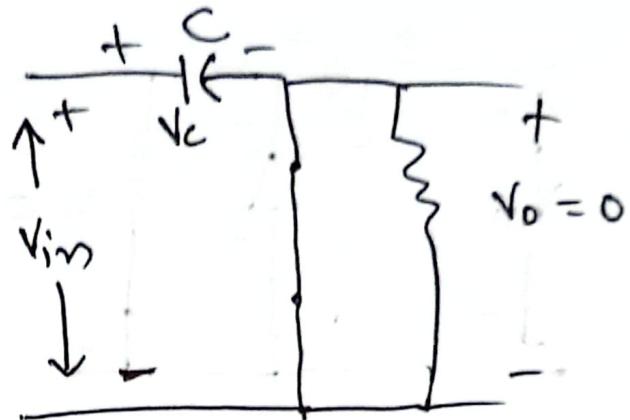

$(2\pi/2)$ half cycle \rightarrow diode short $2\pi/2$ $\pi\pi/2$ $(3\pi/2)$ half-cycl \rightarrow capacitor charge $2\pi/1$



For (-)^{ve} half cycle,

$$+V_{in} + V_C + V_o = 0$$



$$\therefore V_o = -V_{in} - V_C$$

$$= -20 - 20$$

$$= -40V$$

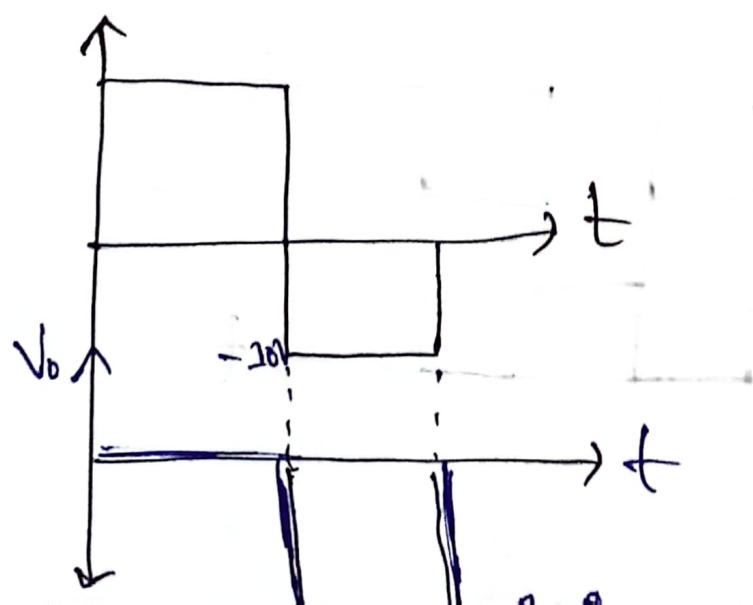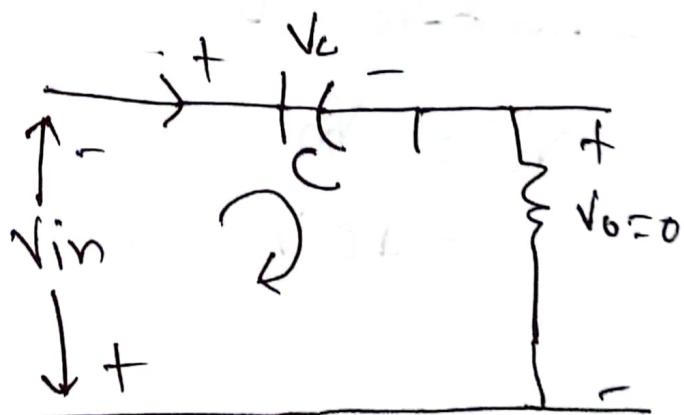

Math-3

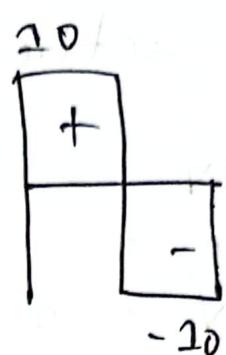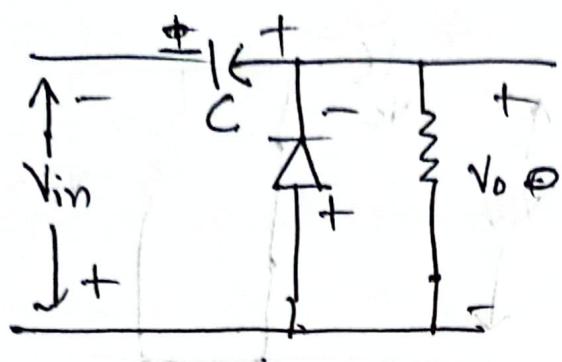


for $(-)^\text{re}$ half cycle,
diode is active,
 $\therefore V_o = 0$



$$+V_{in} - V_C = 0 \\ \therefore -V_C = V_{in} \\ = 20 \text{ V}$$

for $(+)^\text{re}$ half cycle,
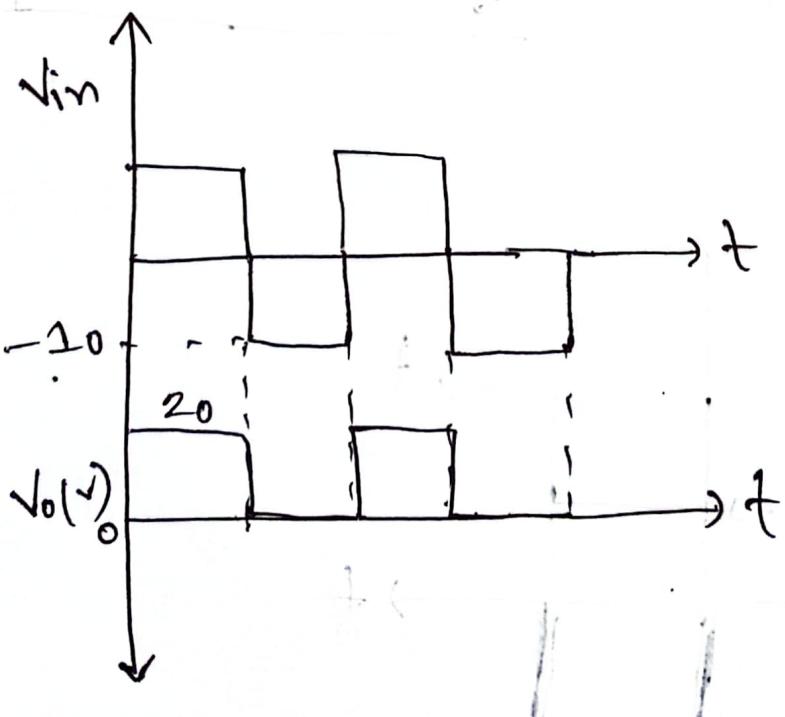
$$-V_{in} - V_C + V_o = 0 \\ \text{or, } V_o = V_C + V_{in} \\ = 10 + 20 \\ = 20 \text{ V}$$



math - 4

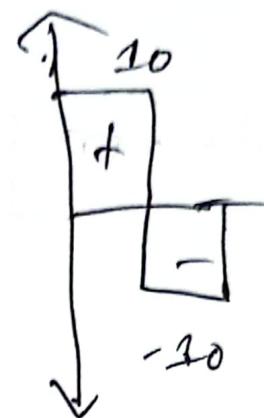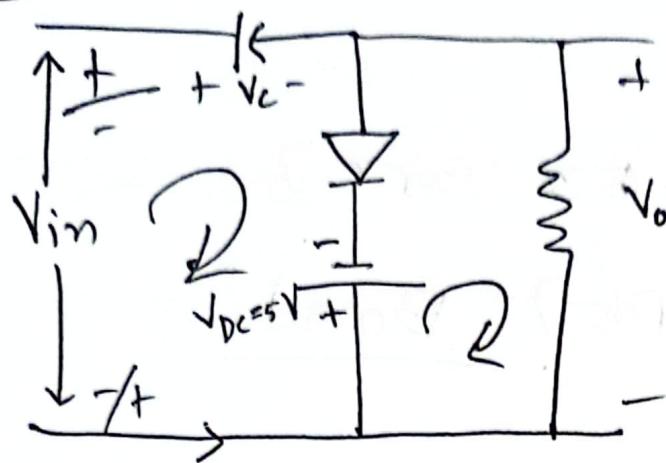

During $(+)^{\text{ve}}$ half,

diode is active (short circuited)

$$V_o = -5V$$

$$-V_{in} + V_c - V_{DC} = 0$$

$$V_c = 5 + \frac{V_{in}}{20V} = 15V$$

During $(-)^{\text{ve}}$ half,

$$+V_{in} + V_c + V_o = 0$$

$$V_o = -V_{in} - V_c$$

$$V_o = -10 - 25$$

$$V_o = -25V$$

